

ELECTRICAL & COMPUTER ENGINEERING
School of Engineering

EGRE 365 – Digital Systems

Homework 4

Name: Luis Barquero

Major: Computer Engineering

Date: 10/31/17

Honor Pledge: *I have neither given nor received any unauthorized help on this lab.*
Signed:

_____ *Luis Barquero* _____

In this Homework, the T-Bird example was modified to include the brake light functionality, alongside the Left and Right turn signal, and the Hazard functionality.

To fully implement the brake light functionality, the following changes were made to the original state transition graph:

Idle (000_000): If the hazard or brakes are on, then the system will transition to LR3, turning on all six lights. Similarly, if the left and right turns are both on, then the system will also enter the LR3 state.

Otherwise, if the left turn signal is activated, then the system will transition to L1, which will turn the first light on the left side, while having the right-side lights off since no brakes have been implemented. Similarly, if the right signal is activated, the system will enter R1, which will have the first light on the right-side on, and the left-side lights off since no brakes were activated.

LR3 (111_111): When the system is the LR3 state, all six lights are on. While in this state, if the brakes have been activated and no turn signal (left = '0' and right = '0') has been detected, then system will remain in the present state.

Otherwise, if the left turn signal is on and the brakes are on, the system enters L4, which will reset left-side lights, while maintaining the right-side lights on, because of the brakes. Similarly, if the right turn signal is on and the brakes are on, the system transitions to R4, which resets the right-side lights and keeps the left-side lights on.

Finally, if the system is LR3 because the hazard lights have been activated, the system will revert back to idle, to simulate the flashing of all six lights.

L1 (001_000): In this state, the first light on the left-side is on, while all the lights on the right-side are off. When the system is in L1, if the hazard lights have been activated, the system will transition to LR3. Otherwise, if no hazard lights have been detected, then the system enters L2 state, which turns the first two lights on the left-side on, and the right-side lights remain off.

Finally, if while in this state the brakes are activated, the system enters L6 state (011_111), which turns on the first two lights on the left-side, but since brakes = '1', all the lights on the right-side will turn on.

L2 (011_000): In this state, the first two lights on the right-side are on, while the lights on the left-side are off. While in this state, if hazard or brakes = '1', the system immediately enters LR3 state. Otherwise, if hazard and brakes = '0', the system transitions to L3 state (111_000), which turns on all lights on the left-side, and the lights on the right-side remain off.

L3 (111_000): In this state, all lights on the left-side are on, and the lights on the right-side are all off. While in this state, if the brakes = '1', the system enters L4 state (000_111), which resets the left-side lights while maintaining the right-side lights all on.

If hazard = '1' or brakes = '1', then the system enters LR3 (111_111), which will turn all six lights on. Otherwise, the system transitions the Idle state (000_000).

L4 (000_111): In this state, the left-side lights have been reset, while the right-side lights are all on since the brakes are still on. While in this state, if brakes = '0', the system enters L1 (001_000). Otherwise, if brakes = '1', the system transitions to L5 (001_111), which turns the first light on the left-side and all three lights on the right-side.

L5 (001_111): L5 will implement the brakes and left-turn signal by having all three lights on the right-side and the first light on the left-side. While in this state, if brakes = '0', the system enters L2 (011_000). On the other hand, if brakes = '1', the system transitions to L6 (011_111), which turns the first two lights on the left-side and all three lights on the right-side.

L6 (011_111): L6 will have the first two lights on the left-side on and all three lights on the right-side on. While in this state, if brakes = '0', the system enters L3 (111_000). Otherwise, if brakes = '1', the system transitions to LR3 (111_111), turning all six lights on.

R1 (000_100): R1 has the first light on the right-side on, and since brakes = '0', the left-side lights are all off. While in this state, if hazards = '1', the system transitions to LR3 (111_111), turning all six lights on. If brakes or hazards = '0', then the system enters R2 (000_110), which turns on the first two lights on the right-side. Finally, if brakes = '1', the system transitions to R6 (111_110), which turns on the first two lights on the right-side, maintaining the three lights on the right-side.

R2 (000_110): R2 has the first two lights on the right-side on, and since brakes = '0', the left-side lights are off. Once again, if hazards or brakes = '1', the system transitions to LR3 (111_111), turning all six lights on. Otherwise, if hazards or brakes = '0', the system will transition to R3 (000_111), turning on all three lights on the right side, and no lights on the left-side.

R3 (000_111): R3 will turn on all three lights on the right-side, and since brakes = '0', left-side lights are off. While in this state, if either hazards or brakes = '1', then system enters LR3 (111_111), turning on all six lights. If, at this state, brakes = '1', the system transitions to R4 (111_000), which resets the right-turn lights. Otherwise, the system goes to idle.

R4 (111_000): R4 will reset the left-turn lights after the brakes have been implemented. While in this state, if brakes = '0', the system enters R1 (000_100), which turns off the left-side lights and turns on the first light on the right-side. Otherwise, if the brakes are still on, then the system enters R5 (111_100), which turns on the first light on the right-side.

R5 (111_100): R5 will turn on the first light on the right-side, and since brakes = '1', all lights on the left-side are on. In this state, if the brakes = '0', then the system will enter R2 (000_110), which will turn off the lights on the left-side and will turn on the first two lights on the right-side. Otherwise, if the brakes = '1', then the system enters R6 (111_110), which turns on the second light on the right-side.

To following is the State Transition Graph illustrating all 14 states:



The T-Bird testbench was also modified to verify that the system transitions to the correct states. First, the system will have the left turn signal activated and then the right signal. Then, the hazards will be activated. From there, the system will turn on the left turn will be activated, and after 20 seconds, the brakes will be activated. Next, the brakes will turn off and after 20 seconds, the left turn also turns on, at which point the right turn signal is activated. After 20 seconds, the brakes turn on and after 60 ns, they will be turn off. After 20 seconds, the right turn signals turns off.

Appendix A

VHDL Code

```

1  --Programmed by: Luis Barquero
2  --Purpose: This program will take the T-Bird's light example, and implement the brakes.
3      --For example, when the brakes are activated, all six lights are on.
4      --When the left or turn signal are on, the lights the lights in the direction of
        the turn
5      -- function as before ? blinking sequentially, the lights opposite the tail lights
6      --are all on continuously.
7
8  library IEEE;
9  use IEEE.std_logic_1164.all;
10
11 ENTITY tbird_lc is
12     PORT (clk          : IN  std_logic;
13           rst          : IN  std_logic;
14           left         : IN  std_logic;
15           right        : IN  std_logic;
16           haz          : in  std_logic;
17           brakes       : in  std_logic;
18           left_tail_lt : OUT  std_logic_vector(3 downto 1);
19           right_tail_lt : OUT  std_logic_vector(1 to 3));
20 END tbird_lc;
21
22 ARCHITECTURE behavior OF tbird_lc IS
23
24     TYPE state_type IS (IDLE, LR3, L1, L2, L3, L4, L5, L6, R1, R2, R3, R4, R5, R6);
25     SIGNAL present_state, next_state : state_type;
26     CONSTANT leftoff : std_logic_vector(3 downto 1) := "000";
27     CONSTANT left1on : std_logic_vector(3 downto 1) := "001";
28     CONSTANT left2on : std_logic_vector(3 downto 1) := "011";
29     CONSTANT left3on : std_logic_vector(3 downto 1) := "111";
30     CONSTANT rightoff : std_logic_vector(3 downto 1) := "000";
31     CONSTANT right1on : std_logic_vector(3 downto 1) := "100";
32     CONSTANT right2on : std_logic_vector(3 downto 1) := "110";
33     CONSTANT right3on : std_logic_vector(3 downto 1) := "111";
34
35 BEGIN
36
37     clocked : PROCESS (clk, rst)
38     BEGIN
39         IF (rst = '1') THEN
40             present_state <= idle;
41         ELSIF (rising_edge(clk)) THEN
42             present_state <= next_state;
43         END IF;
44     END PROCESS clocked;
45
46     nextstate : PROCESS (present_state, left, right, haz, brakes)
47     BEGIN
48         CASE present_state IS
49             WHEN idle => --(000_000). Idle will have all lights turned off.
50                 IF (haz = '1' OR (left = '1' AND right = '1') OR brakes = '1') THEN
51                     next_state <= LR3;
52                 ELSIF (left = '1') THEN
53                     next_state <= L1;
54                 ELSIF (right = '1') THEN
55                     next_state <= R1;
56                 ELSE
57                     next_state <= idle;
58                 END IF;
59
60             WHEN LR3 => --(111_111). LR3 will have all six lights(all 3 from left side and
                all 3 from right side).
61                 IF (left = '1' AND brakes = '1') THEN
62                     next_state <= L4;
63                 ELSIF (right = '1' AND brakes = '1') THEN
64                     next_state <= R4;
65                 ELSIF ((left = '0') AND (right = '0') AND (brakes = '1')) THEN
66                     next_state <= present_state;
67                 ELSE

```

```

68     next_state <= idle;
69     END IF;
70
71     WHEN L1 => --(001_000). L1 will implement the first left light, with the right
lights off because of no brakes.
72         IF(haz = '1') THEN
73             next_state <= LR3;
74         ELSIF (brakes = '1') THEN
75             next_state <= L6;
76         ELSIF (haz = '0') THEN
77             next_state <= L2;
78         END IF;
79
80     WHEN L2 => --(011_000). L2 will implement the first two left light, with the
right lights off because of no brakes.
81         IF(haz = '1' OR brakes = '1') THEN
82             next_state <= LR3;
83         ELSIF (haz = '0' AND brakes = '0') THEN
84             next_state <= L3;
85         END IF;
86
87     WHEN L3 => --(111_000). L3 will have all 3 lights from left side, with the right
side lights off because of no brakes.
88         IF(brakes = '1') THEN
89             next_state <= L4;
90         ELSIF (haz = '1' OR brakes = '1') THEN
91             next_state <= LR3;
92         ELSE
93             next_state <= idle;
94         END IF;
95
96     WHEN L4 => -- (000_111) Left and Brakes. L4 will reset the left turn lights
after all three have been lit when the brake has been activated.
97     IF (brakes = '0') THEN
98         next_state <= L1;
99     ELSIF (brakes = '1') THEN
100         next_state <= L5;
101     END IF;
102
103     WHEN L5 => --(001_111) Left and Brakes. L5 will have the first left light on and
all the right lights on, because of the brakes.
104     IF (brakes = '0') THEN
105         next_state <= L2;
106     ELSIF (brakes = '1') THEN
107         next_state <= L6;
108     END IF;
109
110     WHEN L6 => --(011_111) Left and Brakes. L6 will have the first two left lights on
and all the right lights on, because of the brakes.
111     IF (brakes = '0') THEN
112         next_state <= L3;
113     ELSIF (brakes = '1') THEN
114         next_state <= LR3;
115     END IF;
116
117     WHEN R1 => --(000_100). R1 will implement the first right light, with the left
lights off because of no brakes.
118         IF(haz = '1') THEN
119             next_state <= LR3;
120         ELSIF (haz = '0' AND brakes = '0') THEN
121             next_state <= R2;
122     ELSIF (brakes = '1') THEN
123         next_state <= R6;
124     END IF;
125
126     WHEN R2 => --(000_110). R2 will implement the first two right lights, with the
left lights off because of no brakes.
127         IF(haz = '1' or brakes = '1') THEN
128             next_state <= LR3;

```



```

129         ELSIF (haz = '0' AND brakes = '0') THEN
130             next_state <= R3;
131         END IF;
132
133         WHEN R3 => --(000_111). R3 will have all 3 lights from right side, with the left
134             side lights off because of no brakes.
135         IF (haz = '1' OR brakes = '1') THEN
136             next_state <= LR3;
137         ELSIF (brakes = '1') THEN
138             next_state <= R4;
139         ELSE
140             next_state <= idle;
141         END IF;
142
143         WHEN R4 => -- (111_000) Right and Brakes. R4 will reset the right turn lights after
144             all three have been lit when the brake has been activated.
145         IF (brakes = '0') THEN
146             next_state <= R1;
147         ELSIF (brakes = '1') THEN
148             next_state <= R5;
149         END IF;
150
151         WHEN R5 => --(111_100) Right and Brakes. L5 will have the first right light on and
152             all the left lights on, because of the brakes.
153         IF (brakes = '0') THEN
154             next_state <= R2;
155         ELSIF (brakes = '1') THEN
156             next_state <= R6;
157         END IF;
158
159         WHEN R6 => --(111_110) Right and Brakes. L5 will have the first two right light on
160             and all the left lights on, because of the brakes.
161         IF (brakes = '0') THEN
162             next_state <= R3;
163         ELSIF (brakes = '1') THEN
164             next_state <= LR3;
165         END IF;
166
167     END CASE;
168 END PROCESS nextstate;
169
170 output : PROCESS(present_state)
171 BEGIN
172     CASE present_state IS
173         WHEN idle => --(000_000)
174             left_tail_lt <= leftoff;
175             right_tail_lt <= rightoff;
176
177         WHEN LR3 => --(111_111)
178             left_tail_lt <= left3on;
179             right_tail_lt <= right3on;
180
181         WHEN L1 => --(001_000)
182             left_tail_lt <= left1on;
183             right_tail_lt <= rightoff;
184
185         WHEN L2 => --(011_000)
186             left_tail_lt <= left2on;
187             right_tail_lt <= rightoff;
188
189         WHEN L3 => --(111_000)
190             left_tail_lt <= left3on;
191             right_tail_lt <= rightoff;
192
193         WHEN L4 => --(000_111)
194             left_tail_lt <= leftoff;
195             right_tail_lt <= right3on;
196
197         WHEN L5 => --(001_111)

```

```

194     left_tail_lt <= left1on;
195     right_tail_lt <= right3on;
196
197     WHEN L6 => --(011_111)
198     left_tail_lt <= left2on;
199         right_tail_lt <= right3on;
200
201     WHEN R1 => --(000_100)
202         left_tail_lt <= leftoff;
203         right_tail_lt <= right1on;
204
205     WHEN R2 => --(000_110)
206         left_tail_lt <= leftoff;
207         right_tail_lt <= right2on;
208
209     WHEN R3 => --(000_111)
210         left_tail_lt <= leftoff;
211         right_tail_lt <= right3on;
212
213     WHEN R4 => --(111_000)
214     left_tail_lt <= left3on;
215     right_tail_lt <= rightoff;
216
217     WHEN R5 => --(111_100)
218     left_tail_lt <= left3on;
219     right_tail_lt <= right1on;
220
221     WHEN R6 => --(111_110)
222     left_tail_lt <= left3on;
223         right_tail_lt <= right2on;
224
225
226     END CASE;
227 END PROCESS output;
228
229 END ARCHITECTURE behavior;

```

```

1  --Programmed by: Luis Barquero
2  --Purpose: Testbench will simulate the T-Bird light example, except there is the
3  inclusion of the brakes
4      --The different states will be: Idle, Left Turn(no brakes), Right Turn(no brakes),
5      Hazards, Left Turn(with brakes),
6      --
7      Right Turn(with brakes).
8
9  library ieee;
10 use ieee.std_logic_1164.all;
11
12 entity tbird_testbench is
13 end tbird_testbench;
14
15 architecture behavior of tbird_testbench is
16
17     signal clk_sig : std_logic := '0';
18     signal rst_sig : std_logic := '0';
19     signal left_sig, right_sig, haz_sig, brakes_sig : std_logic;
20     constant Tperiod : time := 10 ns;
21
22 begin
23
24     process(clk_sig)
25     begin
26         clk_sig <= not clk_sig after Tperiod/2;
27     end process;
28
29     rst_sig <= '0', '1' after 2 ns, '0' after 4 ns;          --Reset Signal
30
31     --Left will be on from 20 to 60 ns(no brake), then it will be on from 140-240 (with
32     brakes from 160-220).
33
34     left_sig <= '0', '1' after 20 ns, '0' after 60 ns, '1' after 140 ns, '0' after 240 ns;
35
36     --Right will be on from 60 to 100 ns(no brake), then it will be on from 240-340 (with
37     brakes from 260-320).
38
39     right_sig <= '0', '1' after 60 ns, '0' after 100 ns, '1' after 240 ns, '0' after 340
40     ns ;
41
42     --Hazard will be on from 100 to 140 ns.
43
44     haz_sig <= '0', '1' after 100 ns, '0' after 140 ns;
45
46     --Brakes will be on from 160 to 220 ns(for left turn with brakes), then it will be on
47     from 260-320 (for right turn with brakes).
48
49     brakes_sig <= '0', '1' after 160 ns, '0' after 220 ns, '1' after 260 ns, '0' after
50     320 ns;
51
52     -- this is the component instantiation for the
53     -- DUT - the device we are testing
54     DUT : entity work.tbird_lc(behavior)
55     port map(clk => clk_sig, rst => rst_sig,
56             left => left_sig, right => right_sig,
57             haz => haz_sig, brakes => brakes_sig);
58
59 end behavior;

```

Appendix B

Simulation Output Waveforms



